# Probing the Thermal Fluctuations in Bulk YBCO Superconductors

Jeremy Massengale Senior Seminar 6 May 2013

### Overview

- Review of Jargon
- Experimental Objective
- YBCO Structure
- Experimental Setup/Procedure
- Polycrystalline Correction
- Experimental vs Theoretical Results
- Conclusion/Future Work

# Jargon

• : Critical Temperature

# Experimental Objective

 Investigate thermal fluctuations in a superconductor

Manifests in resistivity/conductivity

# Goals to achieve Objective

- Measure R(T) in sample
- Convert R into
   Accounts for indirect current paths and possibly high contact resistance between SC grains
- Compare experimental ( ) with theoretical predictions
- Determine of sample


### YBCO Structure

Yttrium barium copper oxide (YBCO)

2 3 7-

- Bulk YBCO is a polycrystal
- SEM imaging of YBCO reveals this polycrystallinity

## YBCO Structure

 

## Goal: Measure R(T) in YBCO

- Supply Current Measure
- Utilize thermocouple to determine T
- Require ~ 10 resolution
   Due to bulk material + superconductor
- Common technique is the 4-pt probe method Resistance measured is that <u>ONLY</u> of the sample

# Review: 4-

# Measuring Sample Temperature

- Utilized a Type-T thermocouple (Copper-Constantan)
- \

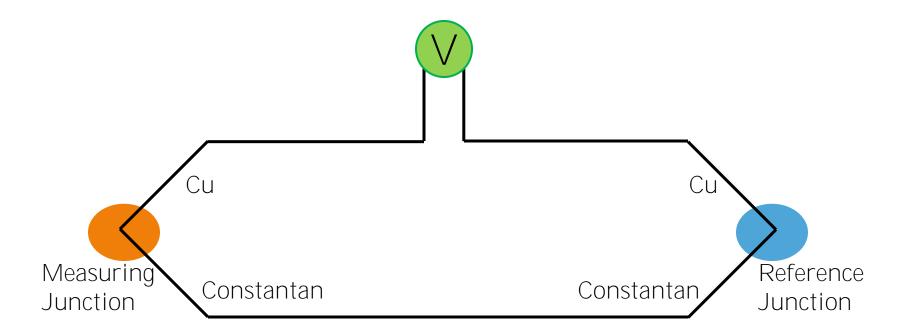


Figure 5. Depiction of a thermocouple used for measuring temperatures.

# Data Acquisition using Logger Pro

- Logger Pro only has millivolt resolution We require microvolt
- To circumvent, we built amplifiers to boost the measured signal
  - With enough gain, able to use Logger Pro for acquisition

# Experimental Setup



Figure 6. Photograph of the full experimental setup.

# Experimental Procedure

- Fix current through sample (dc)
- Cool to LN temperature
- Sample every 2 seconds as sample warms
- =

# Determining Temperature

 Used interpolation to "estimate" a functional relationship between measured voltage and what the corresponding temperature should be.

# Interpolated T vs V

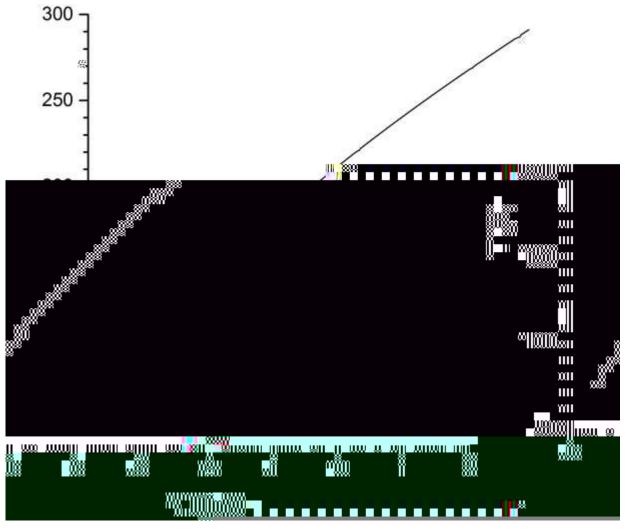


Figure 7. Plot of interpolated T vs

# 35 -30 $\infty$ 0000

Figure 8. Plot

#### Goal: Convert R into

Want to extract from the bulk measurement


• ( ) = 
$$\frac{1}{}$$
 ( ( ) +


• accounts for c@BD40BD5}\text{\text{\$\T}}\ 33er6.62 351.07 Tm()]\text{\$\T}\text{\$\T}



# Polycrystalline Correction

• Fit background data of the form:

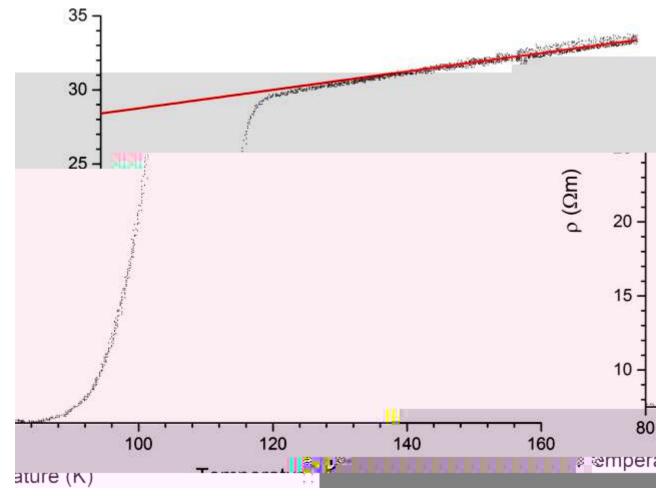

 


## Goal: Determine

### Theoretical Model

• 
$$() = - (1 + - )^{-\frac{1}{2}}$$

• =

## Goal: Experimental () vs Theoretical Prediction

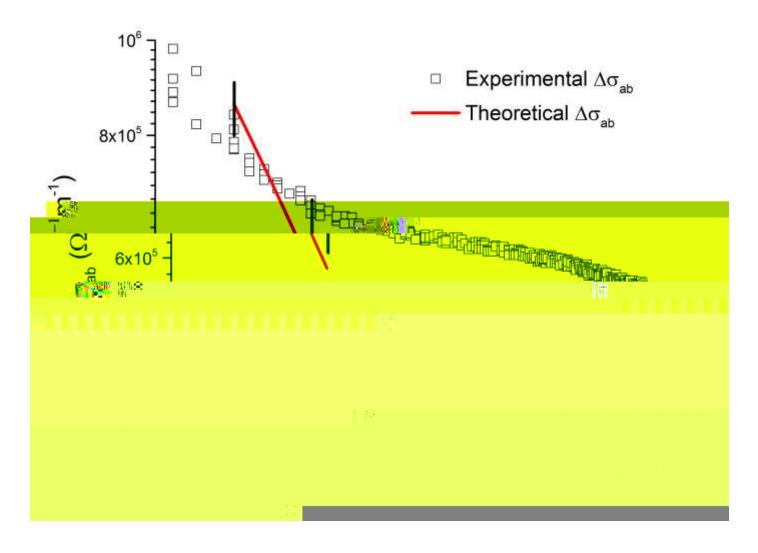


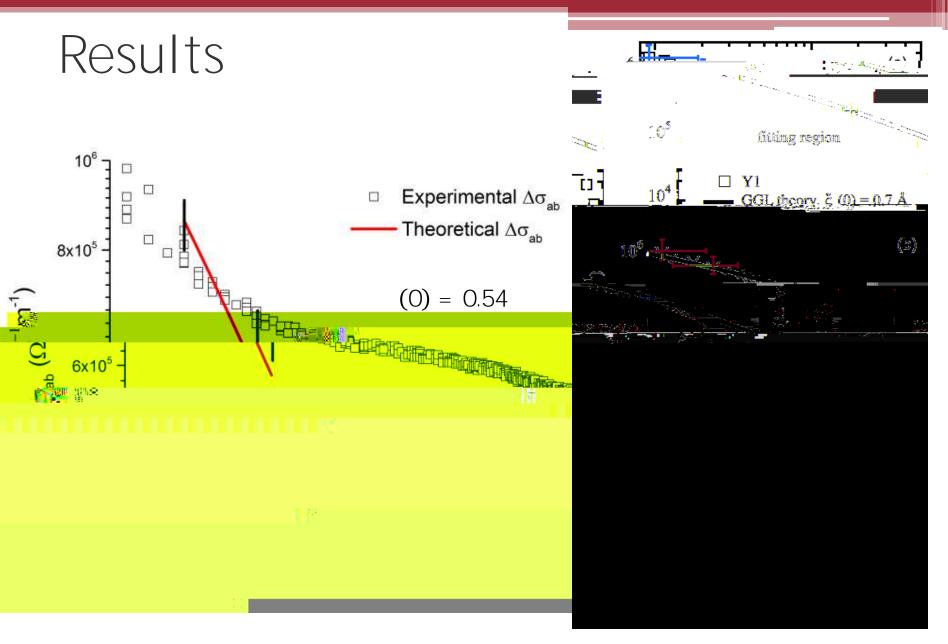


Figure 12. Comparison of our results (left) with Coton et al (right).
 
#### Conclusions


- Built a setup capable of measuring R and T of a YBCO sample.
- Able to observe thermal fluctuations via ( ) deviating from linear background/rounded transition.
- Able to determine




 
### References

- Bhattacharya, R.N., High Temperature Superconductors. (Wiley-VCH Weinheim, Germany, 2010). See chapter 1 in particular.
- Kittel, C., Introduction to Solid State Physics, 8th Edition. (John Wiley and Sons, New Jersey, 2005). P. 259-275.
- Annett, James F., Superconductivity, Superfluids and Condensates. (Oxford University Press, New York, 2004). See Chaps. 3 and 4 in particular.



## Ginzburg-Landau Theory

- Characterizes SC transition based on macroscopic properties
- Introduces
- Developed a spatially varying
   Phenomenological parameters (function of T)
   Density of Cooper-Pairs
- Results in dissipation less current flow
- Concept of a coherence length

### YBCO Structure

• The crye ß

# Amplifier for the Superconductor

- Non-inverting amplifier to measure
- Opted for a G = 1000
- 3dB = 10 Hz



Figure 9. Schematic of the non-inverting amplifier used to measure sample resistance.

# Why G = 1000?

- Want to avoid heating the sample, so we fix current
- fixed, sample resistance fixes
- An appropriate voltage gain chosen to yield full range of Logger Pro's ADC

Voltages represented as a 12 bit binary number (0-4096) Want variations in signal to cover this full range

## Thermocouple Amplifier

- Difference amplifier to measure
- No electrical isolation of components required
- Opted for a G = 750

•

